

# Contents

0.1	Assessment . . . . .	2
<b>1</b>	<b>Lecture Notes</b>	<b>3</b>
1.1	Bits, Bytes and Binary . . . . .	3
1.1.1	Structured Computer Organization . . . . .	3
1.1.2	Unsigned Number in Binary . . . . .	3
1.1.3	Converting Decimal to Binary . . . . .	3
1.1.4	Least and Most Significant Bits . . . . .	3
1.1.5	Conversions . . . . .	4
1.1.6	Negative Numbers . . . . .	4
1.2	Logic Gates . . . . .	4
1.2.1	Logic Functions . . . . .	4
1.2.2	Logic Function Implementation . . . . .	5
1.3	Binary Arithmetic . . . . .	5
1.3.1	Equivalent Circuits . . . . .	5
1.3.2	Overflow . . . . .	5
1.3.3	Full Adder . . . . .	5
1.3.4	Binary Adder . . . . .	5
1.4	Combination Logic . . . . .	6
1.4.1	Combinational Circuits . . . . .	6
1.4.2	Timing Diagram . . . . .	6
1.5	Flip-flops . . . . .	6
1.5.1	D Flip Flop . . . . .	6
1.5.2	Flip-Flops Vs Latches . . . . .	6
1.6	Shift Registers . . . . .	6
1.6.1	Combinational vs Sequential Circuits . . . . .	6
1.6.2	Registers . . . . .	7
1.7	Counters . . . . .	7
1.8	State Machines . . . . .	7
1.8.1	State diagram . . . . .	7
1.8.2	State tables . . . . .	7
1.8.3	State encoding . . . . .	8
1.9	ALUs and Memory . . . . .	8
1.9.1	Parts of a CPU . . . . .	8
1.9.2	Registers . . . . .	8
1.9.3	Buses . . . . .	8
1.9.4	Data Path . . . . .	8
1.10	CPU Control Unit . . . . .	8
1.10.1	Control Unit . . . . .	8
1.11	AVR Introduction . . . . .	9
1.11.1	Instructions . . . . .	9
1.12	Instruction Set Architecture . . . . .	9
1.12.1	Instruction Set Architecture (ISA) . . . . .	9

**Contributors:**

- Daniel Fitz (Sanchez)

## **0.1 Assessment**

- Online Quizzes (10% = Best 10  $\times$  1%)  
Due Mondays at 8am
- Mid-semester exam (10% or 20%)  
Saturday (centrally scheduled - sometime week 5 to 7)  
Multiple-choice, open-book
- Prac Exam (Pass/Fail)  
Held during Monday/Wednesday Learning Lab sessions in week 6  
You must pass in order to pass the course
- Project (20%)  
Develop a microcontroller program
- Final Exam (50% or 60%)  
Short answer, problem solving, open-book

# Chapter 1

## Lecture Notes

### 1.1 Bits, Bytes and Binary

#### 1.1.1 Structured Computer Organization

**Level 5:** Problem-oriented language level

**Level 4:** Assembly language level

**Level 3:** Operating system machine level

**Level 2:** Instruction set architecture level

**Level 1:** Microarchitecture level

**Level 0:** Digital Logic level

#### 1.1.2 Unsigned Number in Binary

Each bit position has a value  $\rightarrow 2^n$  (starting at zero). Add all values of the positions together and that's unsigned value.

#### 1.1.3 Converting Decimal to Binary

- Method 1  
rewrite  $n$  as sum of powers of 2 (by repeatedly subtracting largest power of 2 not greater than  $n$ )  
Assemble binary number from 1's in bit positions corresponding to those powers of 2, 0's elsewhere
- Method 2  
Divide  $n$  by 2  
Remainder of division (0 or 1) is next bit  
Repeat with  $n = \text{quotient}$

#### Note 1: Example

Convert 53 to binary

$$\begin{array}{l} \frac{53}{2} = 26 \text{ rem } 1 \Rightarrow 1 \\ \frac{26}{2} = 13 \text{ rem } 0 \Rightarrow 0 \\ \frac{13}{2} = 6 \text{ rem } 1 \Rightarrow 1 \\ \frac{6}{2} = 3 \text{ rem } 0 \Rightarrow 0 \\ \frac{3}{2} = 1 \text{ rem } 1 \Rightarrow 1 \\ \frac{1}{2} = 1 \text{ rem } 1 \Rightarrow 1 \end{array}$$

$\therefore 53 \equiv 0b110101$

#### 1.1.4 Least and Most Significant Bits

**Most Significant Bit (MSB):** Bit that's worth the most, the left-most bit

**Least Significant Bit (LSB):** Bit that's worth the least, the right-most bit

#### Note 2: Radices

- **Radix:** number system base
- A radix- $k$  number system  
 $k$  different symbols to represent digits 0 to  $k - 1$   
Value of each digit is (from the right)  $k^0, k^1, k^2, k^3, \dots$
- Often convenient to deal with
  - Octal** (radix-8) - Symbols: 0, 1, 2, 3, 4, 5, 6, 7  
*One octal digit corresponds to 3 bits*
  - Hexadecimal** (radix-16) - Symbols: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F  
*One hexadecimal digit corresponds to 4 bits (useful)*

### Note 3: Radix Identification

- Hexadecimal
  - Leading 0x (C, Atmel AVR)
  - Trailing h (Some assembly languages)
  - Leading \$ (Atmel AVR Assembly)
- Octal
  - Leading 0 (C, Atmel AVR)
  - Trailing q (Some assembly languages)
  - Leading @ (Some assembly languages)
- Binary
  - Leading 0b (Atmel AVR Assembly, Some C)
  - Trailing b (Some assembly languages)
  - Leading % (some assembly languages)

## 1.1.5 Conversions

Easiest to convert from most formats to binary then to the desired format.

### Octal

**From Binary:** Group bits into series of 3 and then convert to decimal (0b010 = 02)

**To Binary:** Convert each octal number to binary and append

### Hex

**From Binary:** Group bits into series of 4 and then convert to hex with overflow being apart of the alphabet (0b1100 = 0xC)

**To Binary:** Convert each hex number to binary and append

### Decimal

**From Binary:** Add together the powers of two at each position  $n$  (0b1010 =  $2^3 + 2^1 = 10$ )

**To Binary:** Starting with LSB, divide by 2 with the remainder being bit value at position. ( $9 = 9/2 = 4\text{rem}1, 4/2 = 2\text{rem}0, 2/2 = 1\text{rem}0, 1/2 = 0\text{rem}1. \therefore 9 = 0b1001$ )

## 1.1.6 Negative Numbers

### Signed Magnitude

Leftmost bit is the sign bit, true is negative and false is positive

### One's Complement

Leftmost bit = sign-bit (as per signed magnitude), true is negative and false is positive. If negative all bits are inverted

### Two's Complement

MSB signifies if negative, true is negative and false is positive. To negate invert all bits and add decimal 1.

■ Allows addition without requiring conversion

### Excess $2^{m-1}$

e.g. for 8 bits, excess-128. Add 128 to the original bit and convert to binary

## 1.2 Logic Gates

**NOT Gate:** Inverts the signal (i.e. input is true, output is false)

**AND Gate:** Output is true only if **all** inputs are true

**NAND Gate:** Opposite of AND, always true unless all inputs are true

**OR Gate:** Output is true when at **least one** input is true

**XOR Gate:** Output is true if only one input is true

### Note 4: XOR Multiple Inputs

For more than 2 inputs, XOR is true if there is an odd number of inputs true. Also referred to as the "odd function"

### 1.2.1 Logic Functions

- Logic functions can be expressed as expressions involving:

variables (literals), e.g. A B X

functions, e.g. +,  $\oplus$ ,  $\bar{A}$

- Rules about how this works called **Boolean algebra**

- Variables and functions can only take on values **0** or **1**

## Conventions

**Inversion:**  $\overline{A}$  (overline of A)

**AND:** dot(.) or implied by adjacency.  $AB = A.B$

**OR:** plus sign.  $OR(A, B, C) = A + B + C$

**XOR:**  $OR(A, B) = A \oplus B = \overline{A}B + A\overline{B}$

**NAND:**  $\overline{ABC}$

**NOR:**  $\overline{A + B}$

## Representations of Logic Functions

There are four representations of logic functions (assume function of  $n$  inputs)

- **Truth Table**

Lists output for all  $2^n$  combinations of in-

puts

- **Boolean Function** (or equation)

Describes the conditions under which the function output is true

- **Logic Diagram**

Combination of logic symbols joined by wires

- **Timing Diagram**

## 1.2.2 Logic Function Implementation

Any logic function can be implemented as the OR of AND combinations of the inputs. Called **sum of products**.

Table 1.1: Boolean Identities


Name	AND Form	OR Form
Identity Law	$1A = A$	$0 + A = A$
Null Law	$0A = 0$	$1 + A = 1$
Idempotent Law	$AA = A$	$A + A = A$
Commutative Law	$AB = BA$	$A + B = B + A$
Associative Law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive Law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption Law	$A(A + B) = A$	$A + AB = AB$
De Morgan's Law	$\overline{AB} = \overline{A} + \overline{B}$	$\overline{A + B} = \overline{A}\overline{B}$

## 1.3 Binary Arithmetic

### 1.3.1 Equivalent Circuits

All circuits can be constructed from NAND and NOR gates

### 1.3.3 Full Adder

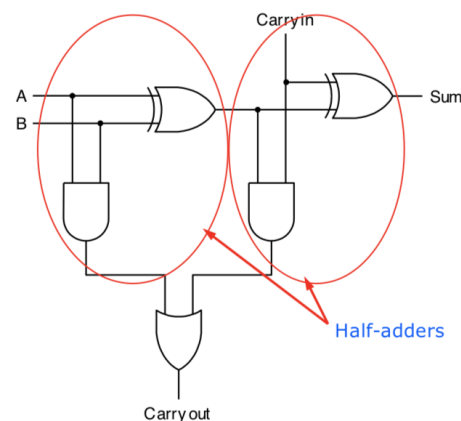


### 1.3.2 Overflow

Overflow with two's complement addition:

- Carry into sign-bit is different to the carry out of the sign-bit
- Equivalently, overflow occurs if
  - Two negatives added together give a positive, or
  - Two positives added together give a negative
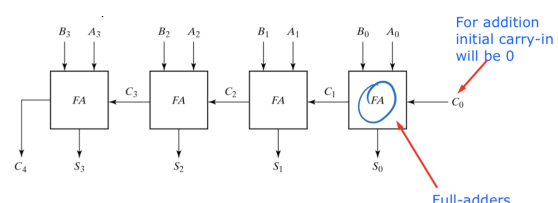
### 1.3.4 Binary Adder

Can cascade full adders to make binary adder. This is a **ripple-carry adder**.



## 1.4 Combination Logic

### 1.4.1 Combinational Circuits

Each output can be expressed as a function of  $n$  input variables. Can write truth table also:

- $n$  input columns
- $m$  output columns
- $2^n$  rows (i.e. possible input combination)

#### Note 5: Multiplexer (or Mux)

- $2^n$  data inputs
- 1 output
- $n$  control (or **select**) inputs - that **select** one of the inputs to be “sent” or “steered” to the output

#### Note 6: Decoder

Converts  $n$ -bit input to a logic-1 on exactly one of  $2^n$  outputs

### 1.4.2 Timing Diagram

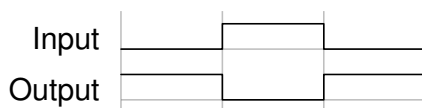


Figure 1.1: Timing Diagram of an inverter

There is a slight delay in logic timings in reality

 


Figure 1.2: Reality of Timing

**Propagation delay:** time for change in input to affect output

**Fall time:** time taken for output to fall from 1 to 0

**Rise time:** time for output to rise from 0 to 1

## 1.5 Flip-flops

### 1.5.1 D Flip Flop

- **D** is input
- **Q** is output
- **CLK** (clock) is control input

Q copies the value of D (and remembers it) whenever CLK goes from 0 to 1 (**rising edge**).

#### Characteristic Table

**Characteristic table** defines operation of flip-flop in tabular form

Table 1.2: D Flip-Flop Characteristic Table

D	Q(t+1)
0	0
1	1

### 1.5.2 Flip-Flops Vs Latches

- The last few slides show **latches**  
These are **level-triggered** devices
- Remember we want to capture the input value at rising **edge** (a short instant)!
- Any devices based on edges are referred to as **flip-flops**

These are **edge-triggered** devices

## 1.6 Shift Registers

### 1.6.1 Combinational vs Sequential Circuits

- **Combinational** Circuits
  - Logic gates only (no flip-flops)
  - Output is uniquely determined by the inputs  
i.e. you'll always get the same output for a given set of inputs
- **Sequential** Circuits
  - Include flip-flops
  - Output determined by current inputs and current **state** (values in the flip-flops)
  - Output can change when clock “ticks” (rising edge)

#### Sequential Circuits

- **State** is value stored in flip-flops

- Output depends on input and state or sometimes just the state
- Next state depends on inputs and state

### Synchronous Sequential Circuit

- Storage elements (flip-flops) can only change at discrete instants of time

### 1.6.2 Registers

- A **register** is a group of flip-flops  
 $n$ -bit register consists of  $n$  flip-flops capable of storing  $n$  bits
- A register is a sequential circuit *without* any combinational logic

### Shift Register

A shift register is a register which is capable of shifting its binary information in one or both directions

## 1.7 Counters

- A **counter** is a multi-bit register that goes through a determined sequence of states (values) upon the application of input pulses
- A counter which follows binary number sequence is a **binary counter**  
 $n$ -bit binary counter has  $n$  flip-flops and can count from 0 to  $2^n - 1$

#### Note 7: State

- Values stored in the flip-flops can be considered the **current state** of the circuit
- D inputs to the flip-flops are the **next state**
- D inputs are some function of the current state and inputs

### Key Points

- Next state is a function of previous state (and possibly inputs)
- Count sequence can be binary numbers but does not have to be  
If it is, counter is a **binary counter**
- Circuits are **synchronous**  
All flip-flops have the same clock

## 1.8 State Machines

- Sequential circuits can also be called state machines  
finite state machines (FSMs)
- State machine has
  - Finite number of possible states
  - Only one **current state**
  - Can **transition** to other states based on inputs and current state

#### Note 8: Types of State Machines

**Mealy Machines:** Outputs depend on current state and inputs

**Moore Machines:** Outputs depend only on current state (flip-flop values)  
Outputs can only change when state changes

### 1.8.1 State diagram

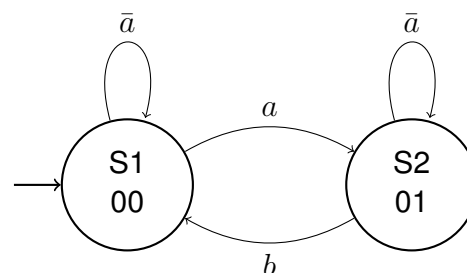


Figure 1.3: Example single input state diagram

*Note: I couldn't figure out how to add the line that is meant to go between the state label and the state number*

### Completeness

Each possible combination of inputs should be addressed **exactly once** for each state. i.e. transition arrows from each state must encompass all possibilities (exactly once)

### 1.8.2 State tables

- State diagrams can also be represented in a state table

Table 1.3: Example State Table

Current State	Input $U$	Next State	Outputs	
			$Q_1$	$Q_2$
S0	0	S3	0	0
S0	1	S1	0	0
S1	0	S0	0	1
S1	1	S2	0	1
S2	0	S1	1	0
S2	1	S3	1	0
S3	0	S2	1	1
S3	1	S1	1	1

Table 1.4: Two-dimensional state table

Current State	Next State		Outputs	
	$\bar{U}$	$U$	$Q_1$	$Q_0$
S0	S3	S1	0	0
S1	S0	S2	0	1
S2	S1	S3	1	0
S3	S2	S0	1	1

### 1.8.3 State encoding

- Must encode each state into flip-flop values
- Choose
  - Number of flip-flops
  - Bit patterns that represent each state
- Ideally, choose state encoding to make combinational logic simple, for both
  - Output logic
  - Next state logic

## 1.9 ALUs and Memory

### 1.9.1 Parts of a CPU

- **Control Unit**
  - Fetches instructions from memory, makes the ALU and the registers perform the instruction
- **ALU**
  - Performs arithmetic and logical operations
- **Registers**
  - High speed memory – stores temporary results and control

### 1.9.2 Registers

Different types of registers

- **Program Counter Register**

Stores the memory address of the next instruction to be fetched

- **Instruction Register**

Contains the current instruction

- **General Purpose Registers**

Contains data to be operated on (e.g. data read from memory), results of operations, ...

Width is CPU word size

Sometimes called the **register file**

### 1.9.3 Buses

**Bus** = Common pathway (collection of “wires”) connecting parts of a computer

Characteristics:

- Can be **internal** to CPU (e.g. ALU to registers)
- Can be **external** to CPU (e.g. CPU to memory)
- Buses have a **width** – number of bits that can be transferred together over a bus

May not always be the same as the word size of the computer

#### Note 9: Arithmetic Logic Unit (ALU)

Does more than adding... **Function / control** input dictates the operation that the ALU is to perform, e.g.

- Addition
- Increment (+1)
- Subtraction
- Bitwise AND
- Bitwise OR

Like adders, ALUs can be made up from 1-bit slices

### 1.9.4 Data Path

- Operands come from register file
- Result written to register file
- Implements routine instructions such as arithmetic, logical, shift
- Width of registers/buses is the CPU word size

## 1.10 CPU Control Unit

### 1.10.1 Control Unit

- Control signals come from the **control unit**



- Control unit must generate the control signals in the right order for a given instruction  
Instruction determined by contents of the **Instruction Register (IR)**

## Data Influencing Control

- Need to know more than what's in the instruction register
- Control unit can't operate without knowing something about the data
- **Status Register**  
Determined by ALU operations  
Stores status of last ALU operation

### Note 10: Status Register

Typically Includes:

**Z:** zero bit – was the last result 0?

**V:** overflow bit – did the last addition/subtraction operation overflow (assuming it was a two's complement operation)?

**C:** carry bit – was a carry out generated?

**N:** negative bit – was the result negative if considered as two's complement (i.e. what's the sign bit)?

- Just build a microarchitecture that implements the ISA

For software writers (machine language programmers and compiler writers)

- Don't need to know (much) about microarchitecture
- Just write or generate instructions that match the ISA

## What makes an ISA?

- Memory modules
  - Issues
    - \* Addressable cell size
    - \* Alignment
    - \* Address spaces
    - \* Endianness
- Registers
- Instructions
- Data types

### Note 11: Addressable Cell Size

- Memory has cells, each of which has a unique address (or cell number)
- Most common cell size is 8 bits (but not always!)  
AVR Instruction memory has 16 bit cells
- Bus is used to transport the content of cell, but sometimes the data bus may be wider

## 1.11 AVR Introduction

### 1.11.1 Instructions

**Opcode** (Operation code): defines the operation

**Operands** : what's being operated on (e.g. particular registers or memory address)

## 1.12 Instruction Set Architecture

### 1.12.1 Instruction Set Architecture (ISA)

**ISA** defines the interface between hardware and software

- ISA is a specification
- **Microarchitecture** is how the control unit is built

For hardware (microarchitecture) designers

- Don't need to know about the high level software

## Bus Sizes

For every doubling of data bus width, remove least significant bit of address bus. e.g. data bus of 32 bits, address bus of  $n-2$  bits, four cells transferred at a time

### Note 12: Alignment

Many architectures require **natural alignment**

### Note 13: Address Spaces

Many microprocessors have a single linear memory address space (**von Neumann architecture**). However, **Harvard architecture** is separate address spaces for instructions and data

#### Note 14: Endianness

- Different machines may support different byte orderings
- **Little endian** - little end (least significant byte) stored first (at lowest address)
- **Big endian** - big end stored first

#### Note 15: AVR I/O Registers

AVR ATmega324A has 224 I/O register addresses to control peripherals and get data to/from them, e.g.

- Timers and counters
- Analog to Digital Converters
- Serial input/output
- General purpose input/output ports
- Three registers associated with each

**DDRx** - Data direction register

**PORTx** - Values to output

**PINx** - Values on the pins

## Registers

Two types of registers:

- General purpose (used for temporary results)
- Special purpose
  - Program Counter (PC)
  - Stack Pointer (SP)
  - Input/Output Registers
  - Status Register (Tanenbaum calls this Program Status Word)

Some other registers are part of the microarchitecture NOT the ISA (e.g. Instruction Register (IR))

## Instructions

Instruction types include:

**Input/Output** - communicate with I/O devices

**Load/Store** - move data from/to memory

**Move** - copy data between registers

**Arithmetic** - addition, subtraction, ...

**Logical** - Boolean operations

**Branching** - for deciding which instruction to perform next